



[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Application Notes](#) > [Amplifier and Comparator Circuits](#) > APP 1163
[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Application Notes](#) > [Digital Potentiometers](#) > APP 1163

Keywords: peak detector, sample and hold, comparators, digital potentiometers, pots, zero droop, droopless

APPLICATION NOTE 1163

Inexpensive Peak Detector Features Droopless Operation

Jan 26, 2001


Abstract: This circuit, which uses a digital potentiometer (pot) and a comparator, features droopless operation that is not normally associated with peak detectors that have traditionally used rectifiers and sample-and-holds (S/H).

Most peak detectors employ a rectifier and a sample-and-hold circuit, which is prone to output droop. In an alternative approach, shown in the figure below, a 5-bit digital potentiometer with a servo loop is used to create an inexpensive peak detector with a logic-level reset input and no output droop.

Comparator control of IC1's chip-select input ensures that the digital potentiometer becomes active only when V_{IN} exceeds the V_{OUT} level currently latched, and R1 ensures that the potentiometer increments upward (rather than downward) as a result. When V_I rises above V_{OUT} , the comparator output (IC2) swings low and selects IC1, allowing the wiper position to increment upwards with each high-to-low transition of the clock (INC*). When V_{OUT} reaches V_{IN} , the comparator output goes high and latches V_{OUT} at that level.

V_{OUT} ranges between the voltage levels connected to the upper and lower extremes of the digital pot (5V and 0V in this case) in 32 equally spaced increments. By reducing this V_{OUT} range, the size of an LSB can be decreased, thereby increasing the output resolution.

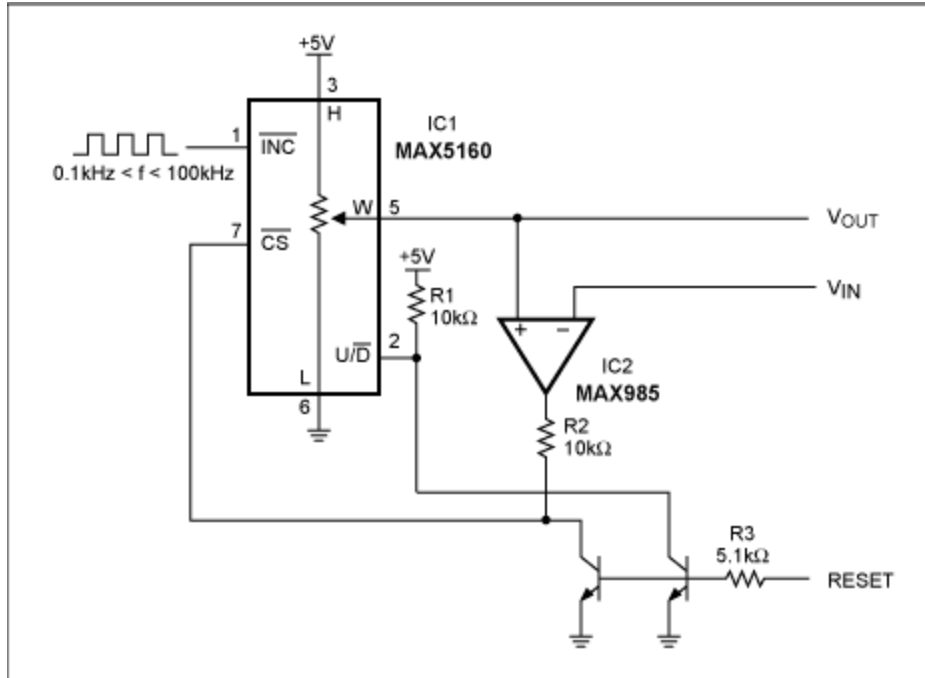Most peak detectors employ a capacitor for holding the output voltage, and the droop (slow change) in V_{OUT} caused by the capacitor's leakage current is particularly noticeable with low frequency or low duty cycle signals. The primary advantage of this circuit is the complete absence of such output droop. It holds the output level indefinitely, making it useful as a long-term memory.



Unlike peak detectors that use a capacitor to hold the output voltage, this design includes a digital potentiometer (IC1) that holds the output level indefinitely, without droop.

*This indicates the inverse of the signal.

A similar version of this article appeared in the May 15, 2000 issue of *Electronic Design*.

Related Parts

MAX5160	Low-Power Digital Potentiometers	Free Samples
MAX985	Micropower, Low-Voltage, UCSP/SC70, Rail-to-Rail I/O Comparators	Free Samples

More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 1163: <http://www.maximintegrated.com/an1163>

APPLICATION NOTE 1163, AN1163, AN 1163, APP1163, Appnote1163, Appnote 1163

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>